

Boolean Algebra and Circuits

Overview

- Truth Tables
- Boolean Functions
- Logic Gates
- Combinatorial Circuits
- Appendix C (4th edition) or Appendix B (5th and 6th edition)

Truth Table

Boolean Operations

- Consider binary variables, A, B
 - Possible values are 0 (FALSE) and 1 (TRUE)
- Different possible inputs with n operands = 2^n
 - 2 binary operands: $2^2 = 4$ different possible inputs
 - 4 binary operands: $2^4 = 16$ different possible inputs

A
0
1

A	B

A	B	C

Boolean Operations

- Consider binary variables, A, B
 - Possible values are 0 (FALSE) and 1 (TRUE)
- Different possible inputs with n operands = 2^n
 - 2 binary operands: $2^2 = 4$ different possible inputs
 - 4 binary operands: $2^4 = 16$ different possible inputs


A
0
1

A	B
0	0
0	1
1	0
1	1

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

Boolean Operations

 
- **AND** operator
- **$A \cdot B$** is true if A **and** B are both true
- Logical product



A	B	$A \cdot B$
0	0	
0	1	
1	0	
1	1	

Boolean Operations

 
- **AND** operator
- **$A \cdot B$** is true if A **and** B are both true
- Logical product



A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

Boolean Operations

 
- **OR** operator
- $A + B$ is true if
 - A is true
 - B is true
 - A and B are both true
- Logical sum



A	B	$A + B$
0	0	
0	1	
1	0	
1	1	

Boolean Operations

 - **OR** operator
- $A + B$ is true if
 - A is true
 - B is true
 - A and B are both true
- Logical sum




A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

Boolean Operations

- **NOT** operator
- \bar{A} is true if A is false
- \bar{A} is false if A is true

A	\bar{A}
0	1
1	0

 

Boolean Operations

- A **Boolean Function** is an algebraic expression consisting of binary variables and the logic operation symbols
- Any Boolean function can be written in terms of **AND, OR, and NOT**
- **Truth table** defines **all** possible outcomes

A	B	$A \cdot B$	$A + B$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

Note on Notation

OR(A,B)

$A + B$

$A \mid B$

$A \mid \mid B$

$A \vee B$

AND(A,B)

$A \cdot B$

$A \& B$

$A \&\& B$

$A \wedge B$

AB

NOT(A)

\bar{A}

$\sim A$

$!A$

$\neg A$

A'

When do we use which?

Boolean Algebra

identity	$A + 0 = A$	$A \cdot 1 = A$
one and zero	$A + 1 = 1$	$A \cdot 0 = 0$
inverse	$A + \overline{A} = 1$	$A \cdot \overline{A} = 0$
commutative	$A + B = B + A,$	$A \cdot B = B \cdot A$
associative	$(A + B) + C = A + (B + C)$	$(A \cdot B) \cdot C = A \cdot (B \cdot C)$
distributive law:	$A \cdot (B + C) = A \cdot B + A \cdot C$	$(A \cdot B) + C = (A + C) \cdot (B + C)$
De Morgan	$\overline{A \cdot B} = \overline{A} + \overline{B}$	$\overline{A + B} = \overline{A} \cdot \overline{B}$

- Rules capture logical reasoning
- Allow for manipulation of expressions




Boolean Algebra

Are two boolean functions equivalent?
Prove it, or find values to show that they are not!

$$A \cdot B \cdot C' + A \cdot C \cdot B' + B \cdot C \cdot A'$$

$$B \cdot (A \cdot C' + C \cdot A')$$

 

Boolean Expression

Derive Boolean Expression

- Consider a logic function with three inputs, A , B , and C , and three outputs, D , E , and F .
 - D is true if at least one input is true
 - E is true if exactly two inputs are true
 - F is true only if all three inputs are true
- Find the Boolean expression for D , E , and F .

Derive Boolean Expression

Find the truth table! *D* is true if at least one input is true

A	B	C	D
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Derive Boolean Expression

Find the truth table! E is true if exactly two inputs are true

A	B	C	D	E
0	0	0	0	
0	0	1	1	
0	1	0	1	
0	1	1	1	
1	0	0	1	
1	0	1	1	
1	1	0	1	
1	1	1	1	

Derive Boolean Expression

Find the truth table! F is true only if all three inputs are true

A	B	C	D	E	F
0	0	0	0	0	
0	0	1	1	0	
0	1	0	1	0	
0	1	1	1	1	
1	0	0	1	0	
1	0	1	1	1	
1	1	0	1	1	
1	1	1	1	0	

Derive Boolean Expression

Inputs			Outputs		
A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1

What are the Boolean expressions for outputs D, E, and F?

Derive Boolean Expression

Inputs			Outputs		
A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1

D is true if at least one input is true

D=

Derive Boolean Expression

Inputs			Outputs		
A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1

F is true only if all three inputs are true

$F =$

Derive Boolean Expression

Inputs			Outputs		
A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1

E is true if exactly two inputs are true

$E =$

Sum of Products, Product of Sums

- **Canonical form** for any logic function
 - Only two levels of gates, one AND, the other OR
 - Possible inversion on the final output.

$$E = (A \cdot B \cdot C') + (A \cdot C \cdot B') + (B \cdot C \cdot A') \quad \text{Sum-of-Product}$$

$$E' = (A' + B' + C) \cdot (A' + C' + B) \cdot (B' + C' + A) \quad \text{Product-of-sum}$$

- Why? Permits an easy/direct/naïve implementation of any Boolean function in hardware

Derive Boolean Expression

- How to derive a Boolean expression
 - Step 1: Write down the truth table
 - Step 2: Find the sum-of-product or product-of-sum
 - Step 3: Simplify it (optional)


Circuits




Logic Gates

- **Logic Gates:** Abstraction for building Boolean expressions in hardware
- Gates are made from **transistors**

Electric Board

 

TRANSISTORS

 


LOGIC GATE



Common Logic Gates

- AND, OR, XOR, and inverted versions

 

Common Binary Operations

- Three other very common operations:

- NAND: Not And
- NOR: Not OR
- XOR: Exclusive OR


A	B	NAND	NOR	XOR
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	0	0	0

- Using AND, OR, NOT, how would you write expressions for each of these functions?

Combinational Circuits


- **Combinatorial circuit:** a circuit that implements a Boolean function

Draw the circuit for $Y = (AB)' + AC$

 


Multiple Inputs

 - Can put > 2 inputs on an AND or OR gate
- Allowed because of the associative law
- Commutative law of Boolean algebra: the ordering of the wires into a AND and OR gates doesn't matter
- Example: 3 input AND gate (*these functions are symmetric*)



Don't Care!

 

Don't Care

Situations where we do not care about the value of an output

- Because another output is true

e.g., If A is true, then $A + B$ is true. We don't need to check B

e.g., if A is false, then $A \cdot B$ is false. We don't need to check B

- Or we don't care about the output for specific input combinations

Don't Care

- Can be easier to specify the truth table
- Write the truth table, marking **X** for “Don't Care”

– Inputs S, A, B

– Output C

– If S is true, output is A

– If S is false, output is B


S	A	B	C
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

S	A	B	C
0	x	0	0
0	x	1	1
0	x	0	0
0	x	1	1
1	0	x	0
1	0	x	0
1	1	x	1
1	1	x	1

S	A	B	C
0	x	0	0
0	x	1	1
1	0	x	0
1	1	x	1

Don't Care

 
- We can also build simpler circuits by letting outputs take on any convenient value
 - Write the truth table for the **middle segment** of BCD to a 7-segment display decoder



A3	A2	A1	A0	m
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	x
1	0	1	1	x
1	1	0	0	x
1	1	0	1	x
1	1	1	0	x
1	1	1	1	x

Don't Care

 - We can also build simpler circuits by letting outputs take on any convenient value
 - Write the truth table for the **middle segment** of BCD to a 7 segment display decoder



$$M = (A_3'A_2'A_1'A_0' + A_3'A_2'A_1'A_0 + A_3'A_2A_1A_0)'$$

A3	A2	A1	A0	m
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	x	x
1	1	x	x	x

Circuit Minimization

- The problem of obtaining the smallest logic circuit (Boolean formula) that represents a given Boolean function or truth table.
- The problem is believed to be ***hard***, but there are effective heuristics (Karnaugh maps, the Quine–McCluskey algorithm).
- Beyond the scope of this course...
 - See Randy H. Katz, "Contemporary Logic Design"

Review and more information

- Truth Tables
- Boolean Functions
- Logic Gates
- Combinatorial Circuits
- The best thing about a Boolean function is that even if you are wrong, you are only off by a bit
- This class covers topics in textbook
 - Appendix C of 4th edition
 - Appendix B of 5th edition