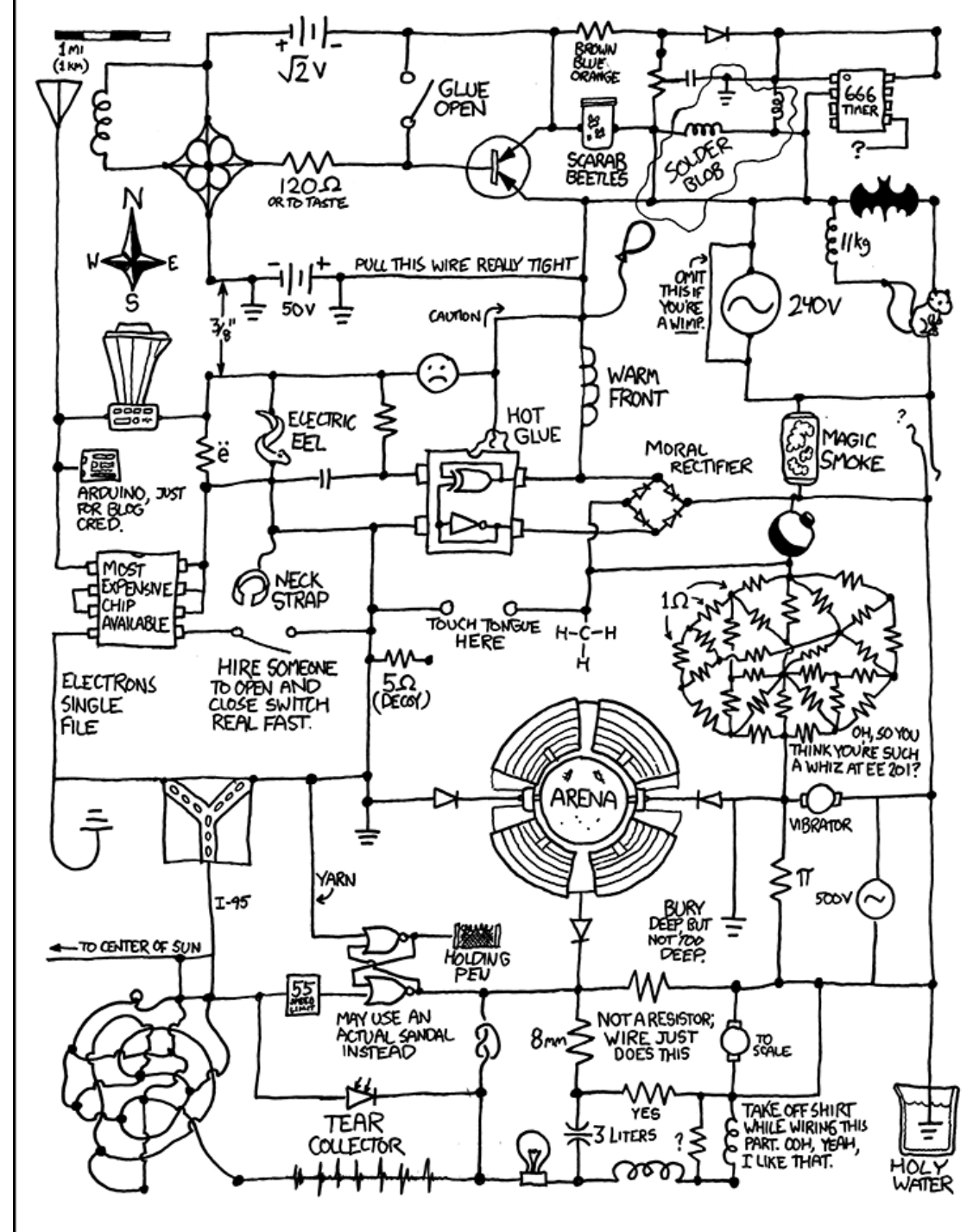



# Combinatorial Circuits



# Overview



- How to build an adder
- Common combinational circuits
  - Decoders and encoders
  - Multiplexors
  - Read-only memory
  - Programmable logic array
  - Arithmetic logic unit

# The Big Picture Again

 
  
# Combinational Circuits

- **Combinational/Combinatorial circuit:** a circuit that implements a Boolean function




# Circuits for Binary Arithmetic

# 1-Bit Half Adder

- Inputs: two bits A and B
- Outputs: sum and carry out

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 
$\text{Sum} = A'B + AB'$   
 $\text{Carry} = AB$



# 1-Bit Half Adder

- Inputs: two bits
- Outputs: sum and carry out


A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1
Sum = A XOR B			
Carry = AB			

 

# 1-Bit Full Adder

- Inputs: two bits (A, B) + carry from the previous bit (C)
- Outputs: sum and carry

C	A	B	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


$$\begin{aligned}\text{Sum} &= C' A' B + C' A B' + C A' B' + C A B \\ &= C' (A' B + A B') + C (A' B' + A B) \\ &= C' (A \text{ XOR } B) + C (A \text{ XOR } B)' \\ &= C \text{ XOR } (A \text{ XOR } B)\end{aligned}$$

$$\begin{aligned}\text{Carry} &= C' A B + C A' B + C A B' + C A B \\ &= C' (A B) + C (A' B + A B') + C (A B) \\ &= (C' + C) A B + C (A \text{ XOR } B) \\ &= A B + C (A \text{ XOR } B)\end{aligned}$$




# Multi-Bit Adder

- Chain together adders!

 

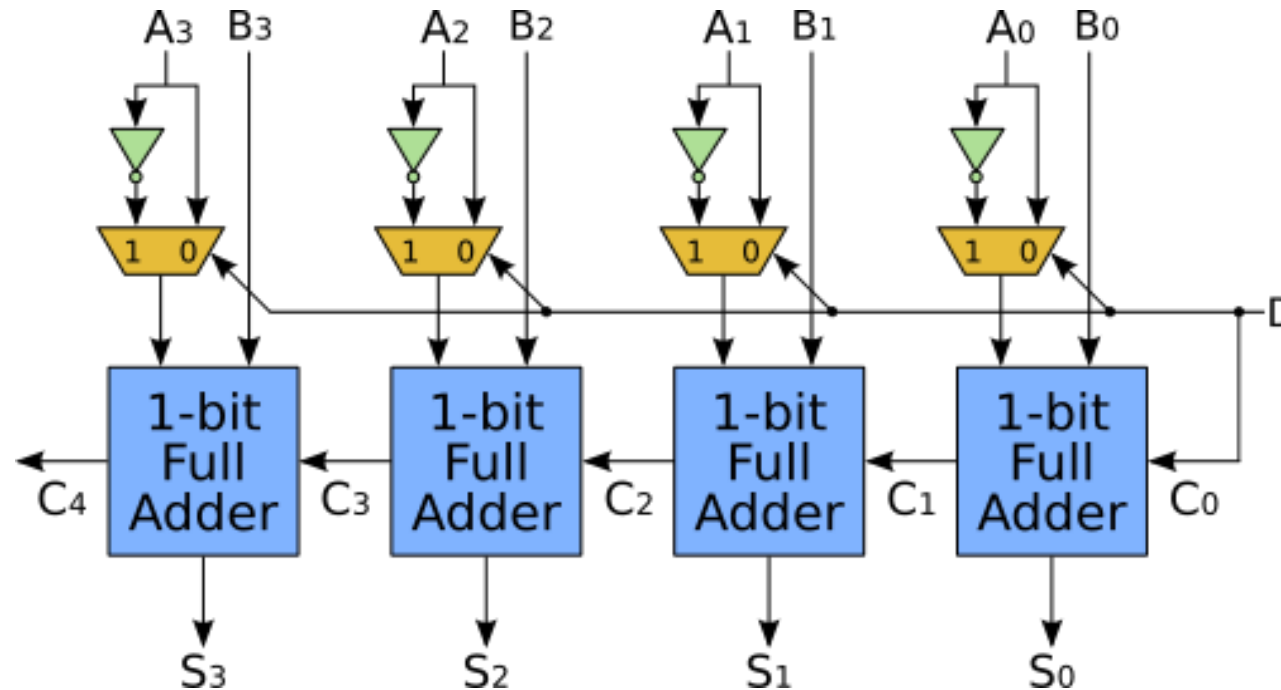
# Multi-bit Subtractor

- $B - A = B + (-A)$
- Inverted bits of A + B. Add one using the first carry in.


 
# Potential Problems?

- Carry must ripple (propagate) through each adder
- The MSB depends on the carry of each preceding bits
- In the case of 32-bit or 64-bit integer, the **delay** is significant




- Solutions: Carry look ahead addition, Carry-save adder (B.6)

# Common Circuits
 
# Decoders

- A **decoder** has  $n$ -bit input and  $2^n$  outputs
- Only one output active for each input combination



a. A 3-bit decoder

Inputs			Outputs							
A2	A1	A0	Out7	Out6	Out5	Out4	Out3	Out2	Out1	Out0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

b. The truth table for a 3-bit decoder

# Encoders

- Opposite of a decoder
  - Output only specified if one input is 1



Assume only one button  
can be pressed at any time

Inputs								Outputs		
$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1



$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$
  
# Multiplexor

- The **Selector**. Use often
  - 2 signals **A**, and **B**, and a selector **S**
  - If **S = 0**, output = **A**
  - Otherwise, output = **B**



$$C = S'A + SB$$


S	A	B	C
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

# Multiplexor


- Can have any number of inputs
  - Given  $n$  signals, need  $\lceil \log_2 n \rceil$  selector inputs
- Three step recipe for building a multiplexor
  - A decoder that generates  $n$  signals
  - An array of  $n$  AND gates to combine the signals
  - A single  $n$  input OR gate to compute the result



# Full adder circuit

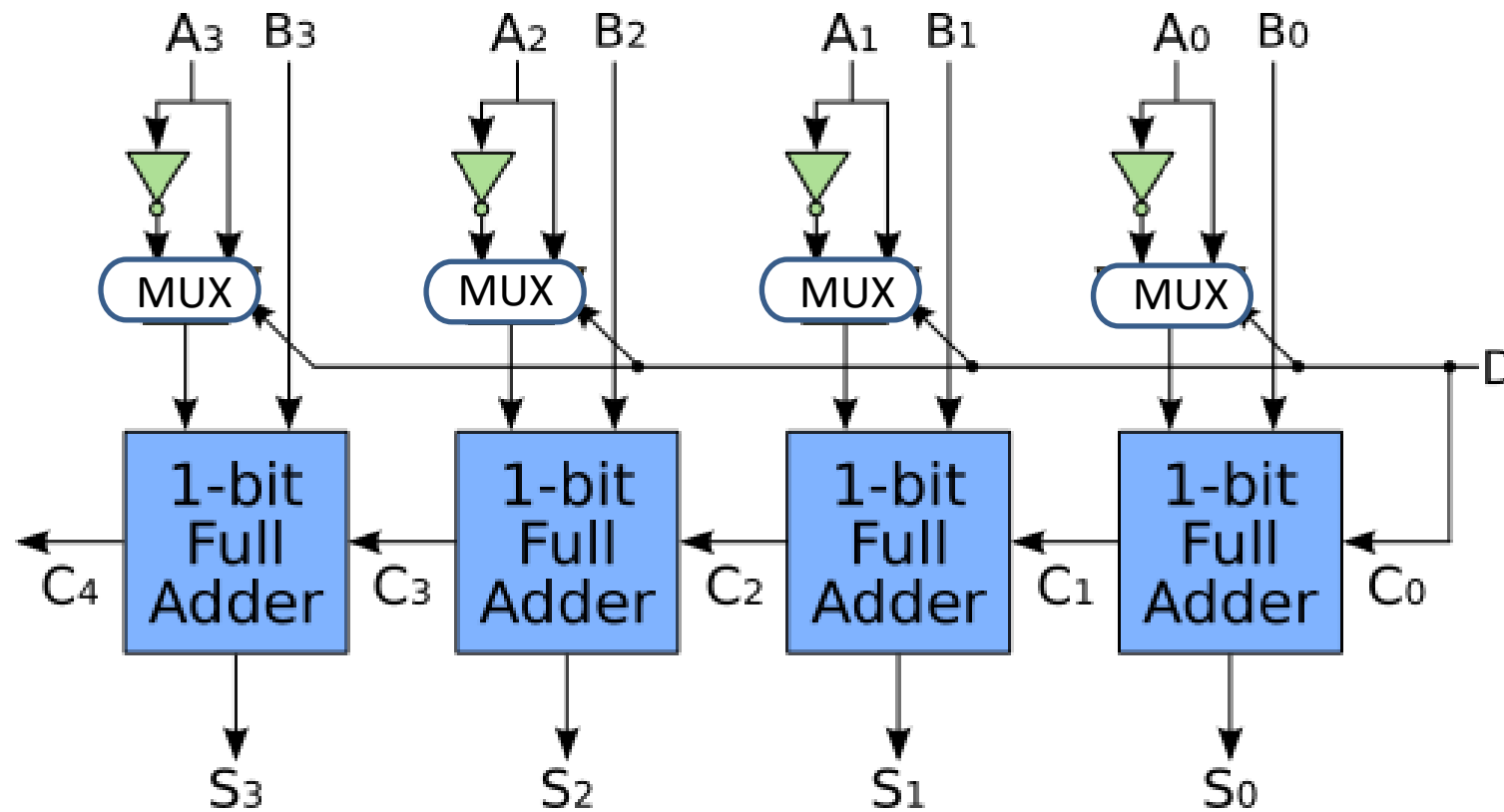



# Multiplexor

 

- Eight different signals (A-H)
- 3-8 Decoder for selecting the inputs
  
# Arrays of Logic Elements

- Many operations need to be done on an entire word (32 bits)
- For instance, a multiplexor that selects one of two words:




# Read-only Memory (ROM)

- Inputs encode the memory address
- Outputs are the contents at each address
- Consider a circuit as a "hardwired" memory

$A_1$	$A_0$	$b_2$	$b_1$	$b_0$
0	0	0	1	1
0	1	0	0	1
1	0	0	0	0
1	1	1	0	0
 
# Programmable Logic Array (PLA)

**Canonical form:** only two levels of gates



- The **AND gates array** is a product term consisting of any number of inputs or inverted inputs
- The **OR gates array** is a sum term consisting of any number of these product terms.

# Programmable Logic Array (PLA)


$$D = A + B + C$$

$$D = (A'B'C + A'BC' + \dots + ABC' + ABC)$$


$$E = (A \cdot B \cdot C') + (A \cdot C \cdot B') + (B \cdot C \cdot A')$$

$$F = A \cdot B \cdot C$$

Inputs			Outputs		
A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1

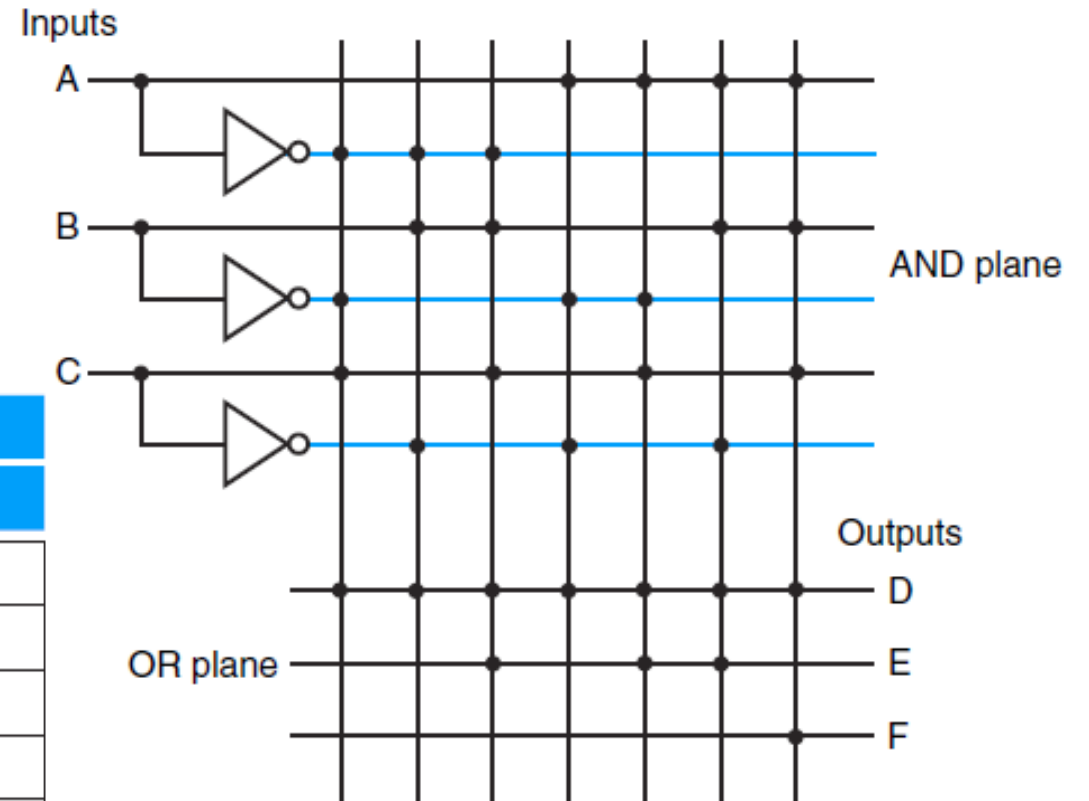


# Arithmetic Logic Unit (ALU)

 


**1-Bit ALU**

Instruction	Ainvert	Binvert	CarryIn	Operation
ADD	0	0	0	2
SUB	0	1	1	2
AND	0	0	x	0
OR	0	0	x	1
NOR	1	1	x	0
SLT	0	1	1	3

# Arithmetic Logic Unit (ALU)

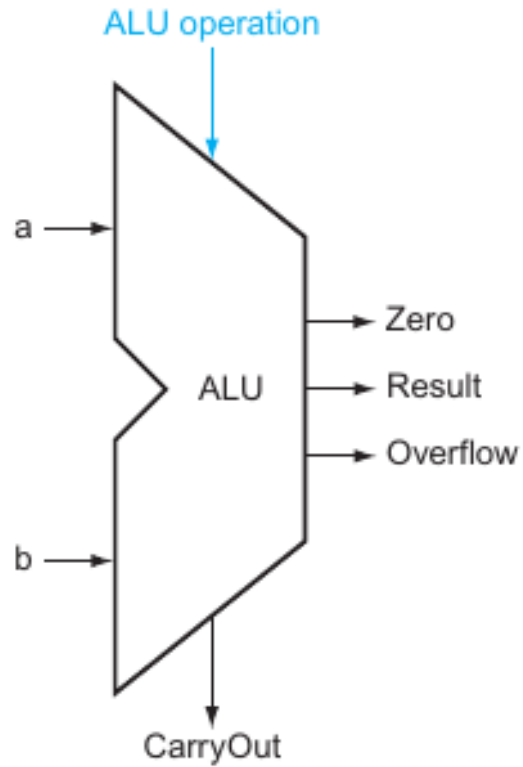

## 32-Bit ALU

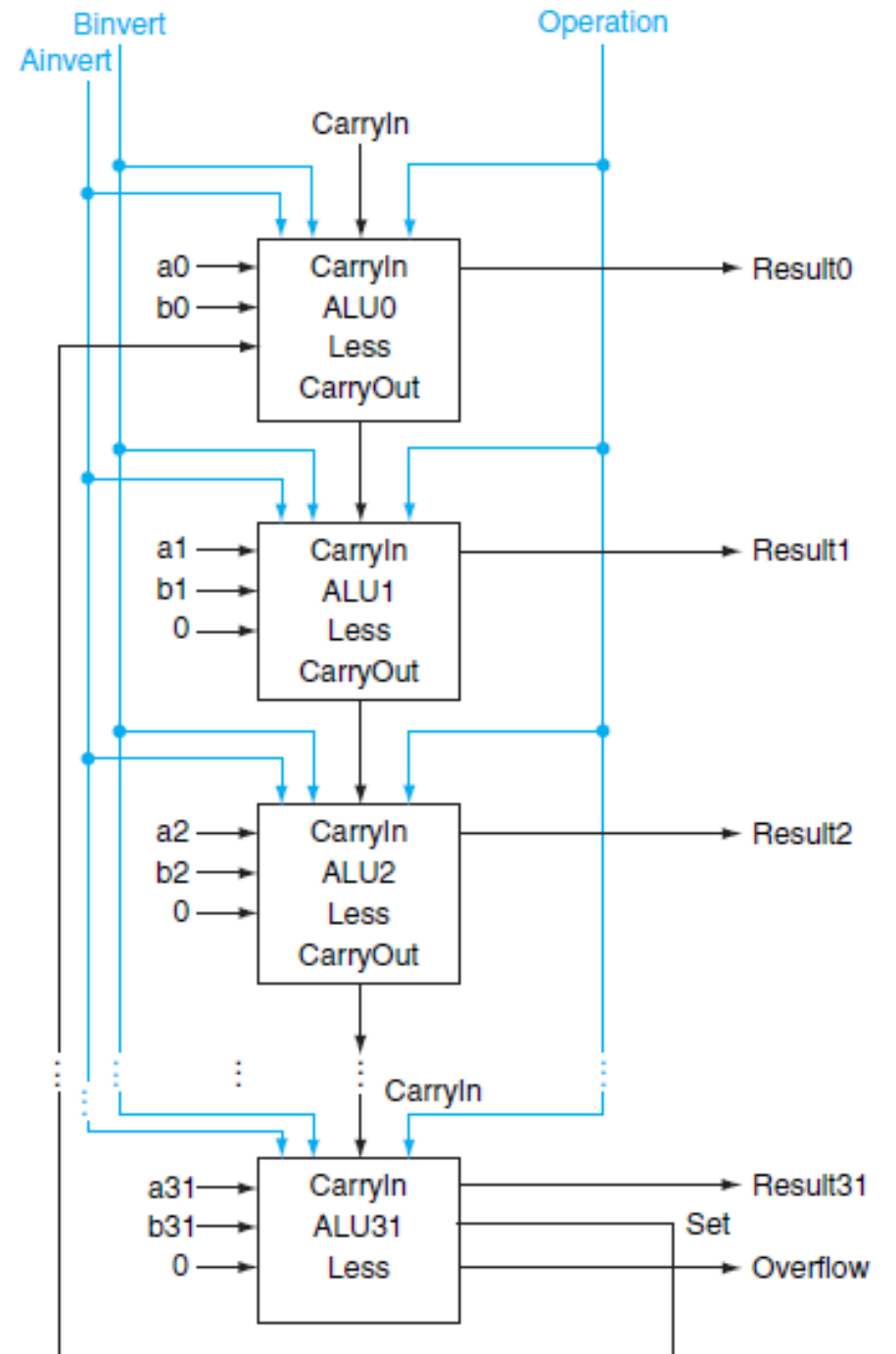



# Review

- Adder
- Common circuits
  - Decoder and Encoder
  - Multiplexor
  - Read-only Memory (ROM)
  - Programmable Logic Array (PLA)
  - Arithmetic Logic Unit (ALU)
- Textbook: Appendix B.8 of 5<sup>th</sup> and 6<sup>th</sup> edition

# Sequential Circuits

# Agenda

- RS Latch
- D Latch
- D Flip flop
- T Flip flop

# Sequential Circuits

- **Combinatorial circuits** have no memory
  - Output is simply a function of inputs
- **Sequential circuits** contain “state”
  - Combinatorial circuits + memory
  - The mechanism for remembering information (i.e., bits) inside the CPU and in the main memory.
  - How to remember things?
    - Write it down
    - **Repeat it to yourself** (sequential circuits style)






# Latch

# RS flip-flop

- Two inputs S and R
  - S = 1, **set** output to 1
  - R = 1, **reset** output to 0
  - S, R are both 0, **hold** the values

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0


R	S	Q	Q'
0	0	Q	Q'
0	1	1	0
1	0	0	1

 

# RS flip-flop


- Problem:
  - When S, R are both 1, **invalid**

R	S	Q	Q'
0	0	Q	Q'
0	1	1	0
1	0	0	1
1	1	invalid	invalid

 
 
# Clocks



- Mechanism for synchronizing inputs and outputs.
- Metronome
- Clock speed is in Gigahertz





  
# Clocks

- Recall that it takes time for combinatorial circuits to produce results.
  - e.g., carry ripple in adder
- Want results to be finished before we store the result somewhere


 
# D Latch


- D for “Data”
- Q records state of D (holds previous value of D while  $C = 0$ )



**SR Latch**
 
# D Latch

- When  $C = 0$ , hold values of  $Q$  and  $Q'$
- When  $C = 1$ ,  $D = 1$ , then set  $Q = 1$ ,  $Q' = 0$
- When  $C = 1$ ,  $D = 0$ , then reset  $Q = 0$ ,  $Q' = 1$
- Impossible for  $R$  and  $S$  to be both 1




# Flip-flop




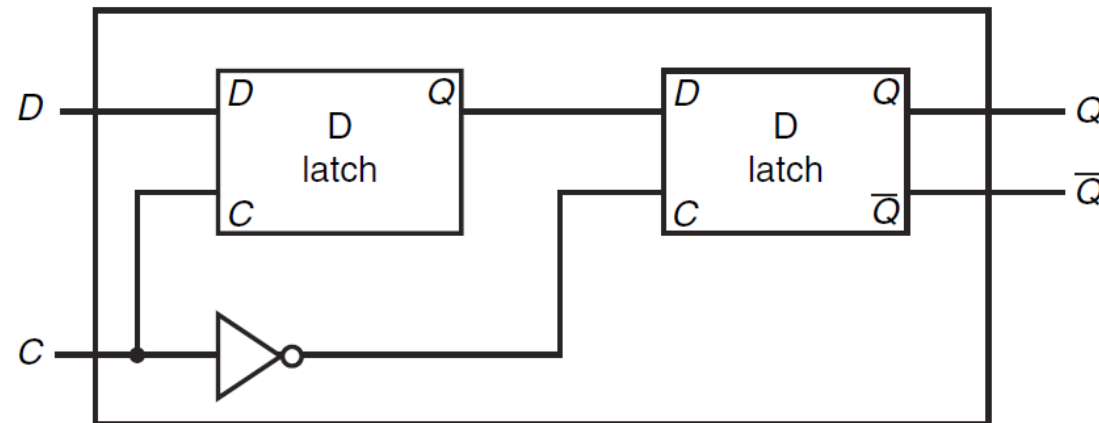
# D flip-flop

- **Two D latches.** One for reading and one for writing
- Mechanism prevents data from being read/write at the same time



- By putting an inverter, change when the **falling edge** is triggered


# D flip-flop

 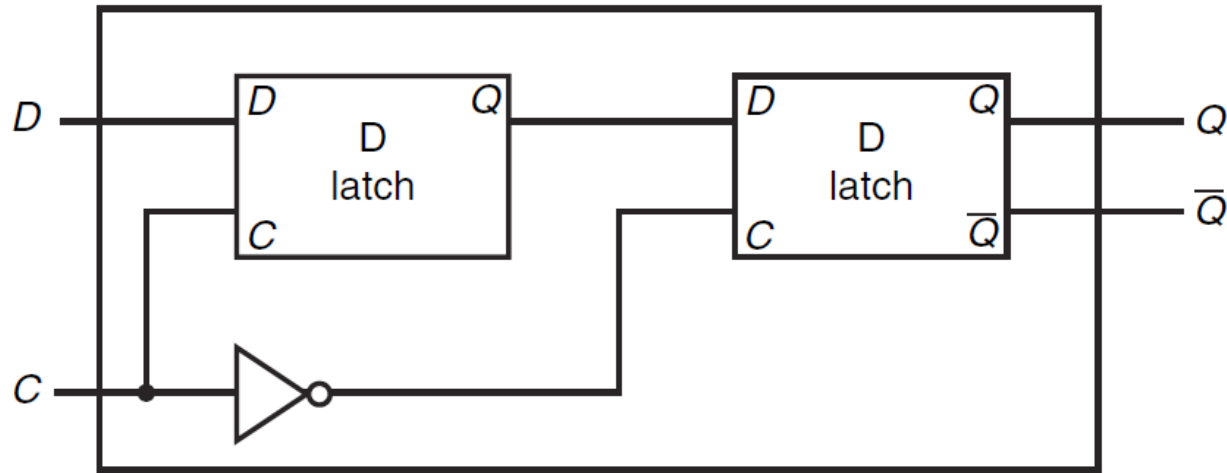


- When  $C = 1$ 
  - write D into the first D latch
  - Q does not change
- When  $C = 0$ 
  - Stop writing D into the first D-latch.
  - The D value from the first D-latch is written into the second D-latch

# D flip-flop

Rising edge D flip-flop

 


Falling edge D flip-flop (small circle)

 
 
# D flip-flop Setup and Hold


- **Setup time:** Input must be stable before the falling clock edge
- **Hold time:** Input must also be stable after clock edge
  - Hold times typically *very small*, or zero




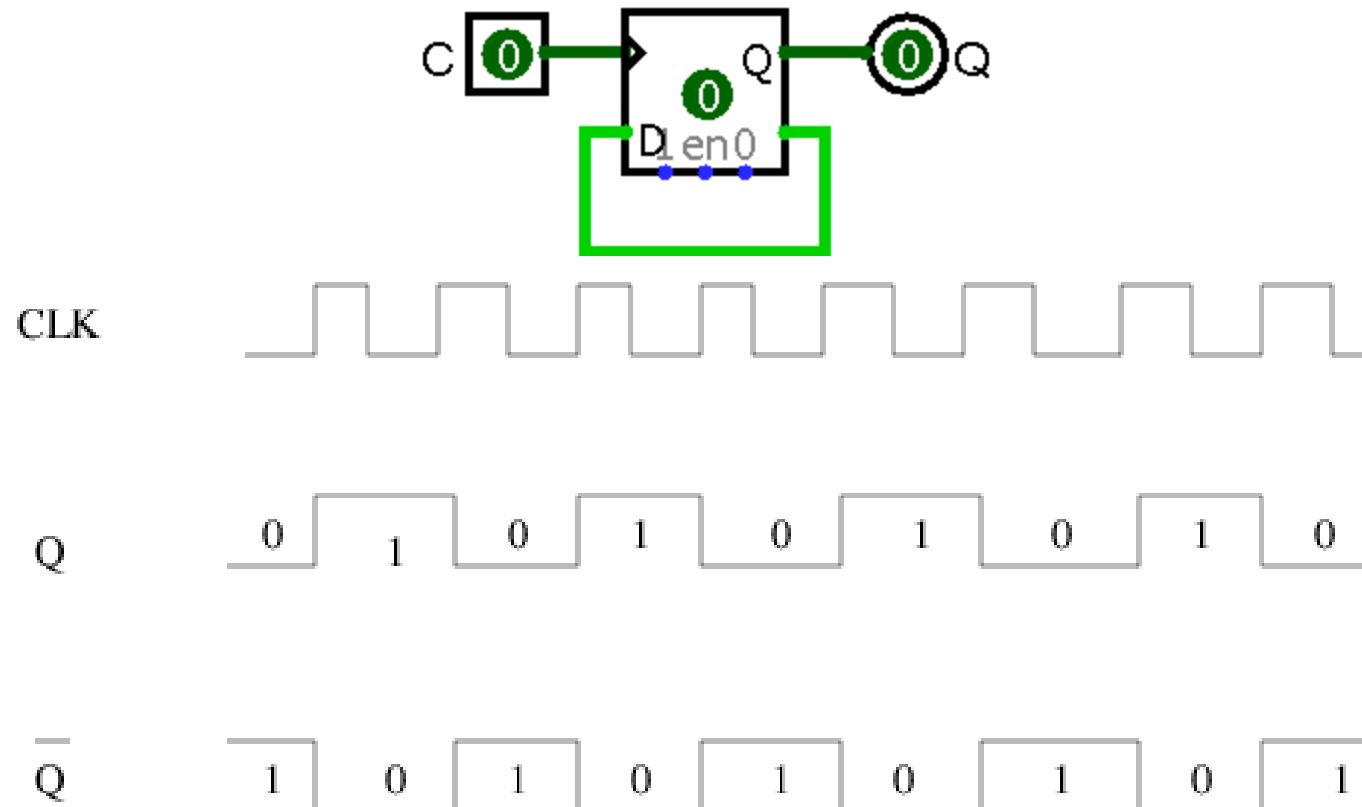
# Toggle Flip Flop

- Hook  $Q'$  up to D, and clock becomes a **toggle**



# Review and more information

- RS Latches
  - D Latch
  - D Flip flop
  - T Flip flop
- 
- Textbook: Appendix B.7 and B.8 of 5th and 6th edition
  - Next topic: Registers (use sequential circuits)