

Multiplication and Division

Agenda

- Multiplication (3.3)
- Division (3.4)


Multiplications

Revisit Integer Multiplication


- $P = A \times B$
 - A : *Multiplicand*
 - B : *multiplier*
 - P : *product*
- $$\begin{array}{r}
 A_{n-1} \dots A_1 A_0 \\
 \times B_{n-1} \dots B_1 B_0 \\
 \hline
 P_{2n-1} \dots P_{n-1} \dots P_1 P_0
 \end{array}$$
- “multiplicand”
“multiplier”
“product”
- Multiplicand is multiplied **by each bit** of the multiplier
 - Each intermediate result is added up to get the final *product*.

Unsigned Binary Multiplication

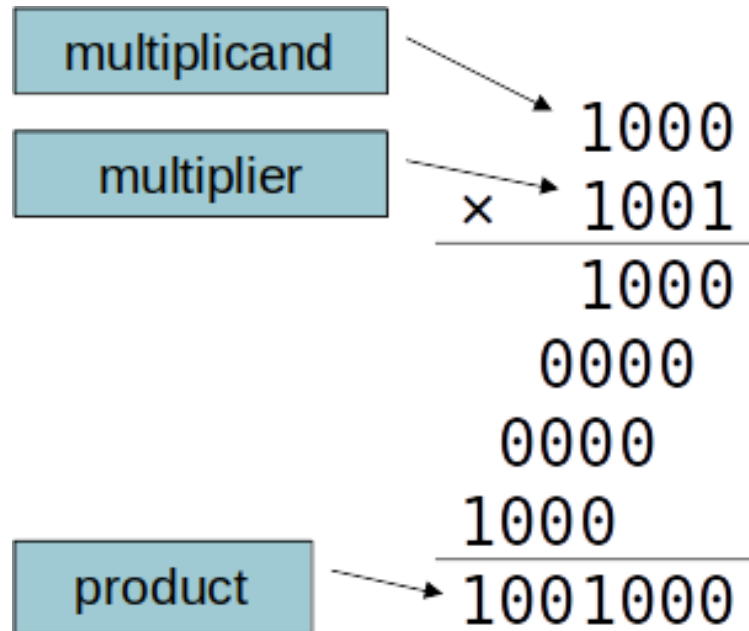- Multiplying each bit is easy because it is either 1 or 0




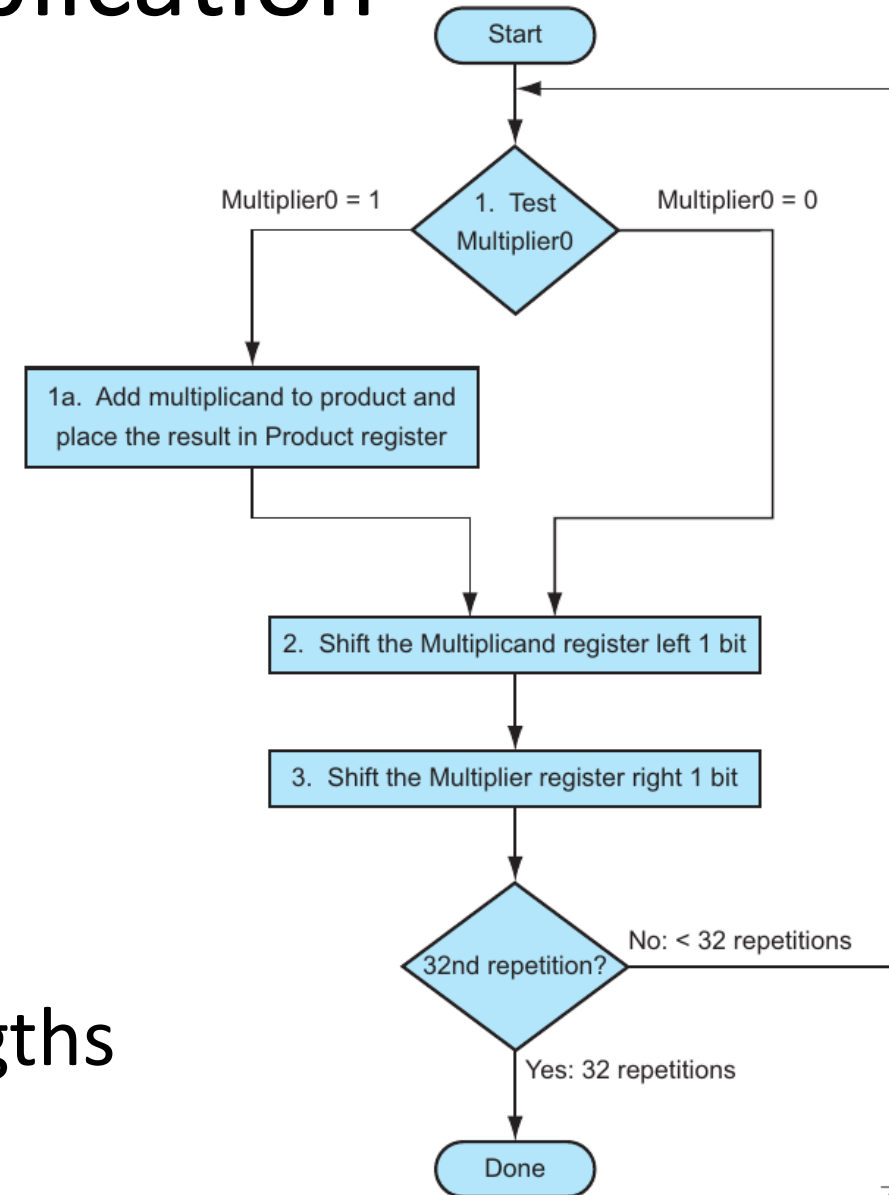- Length of product = sum of operand lengths





Unsigned Binary Multiplication

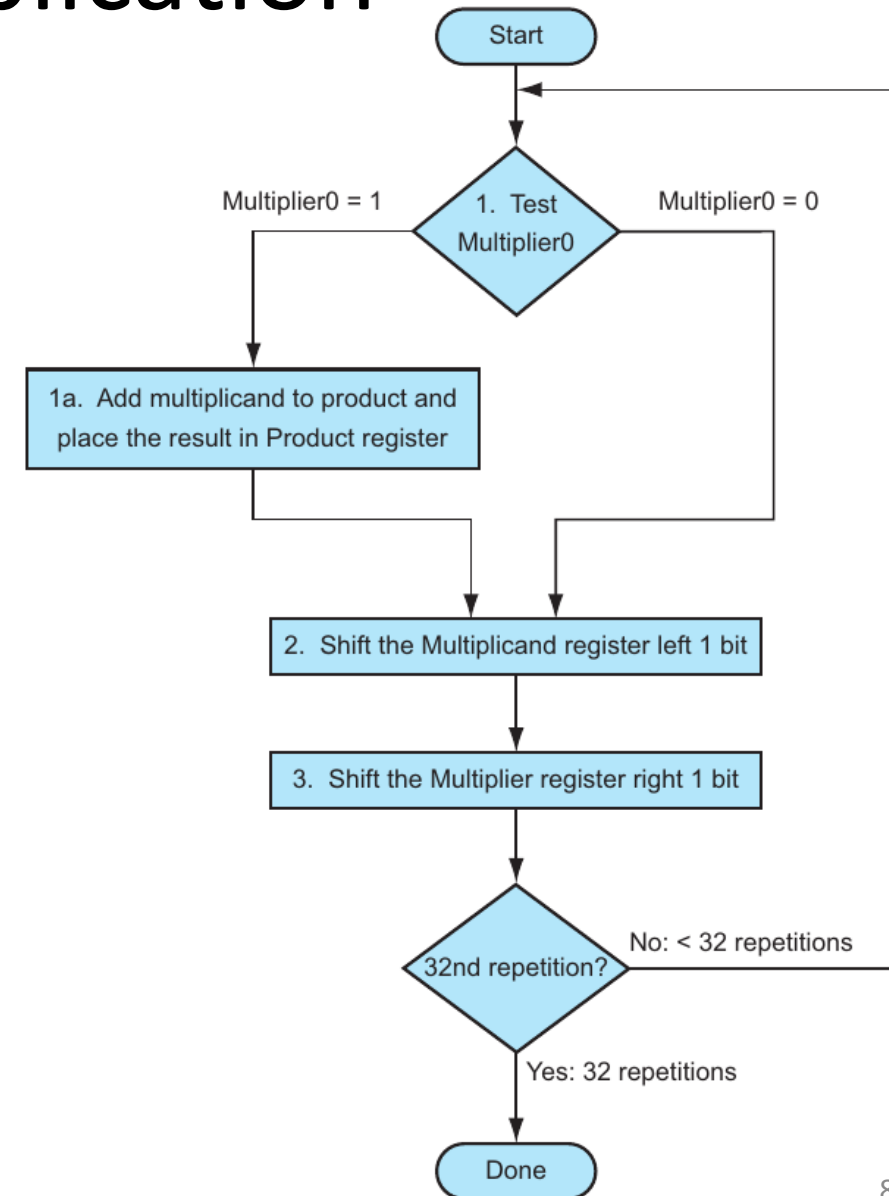- **Multiplicand:** 64 bits shift (left) register
- **Multiplier:** 32-bit shift (right) register to read the LSB on each add
- **Product:** 64-bit register
- **Adder circuit:** 64-bit ALU
- **Counter:** keep track of how many times we shift (in this case can be 5 bit counter register)



Simple Multiplication Circuit

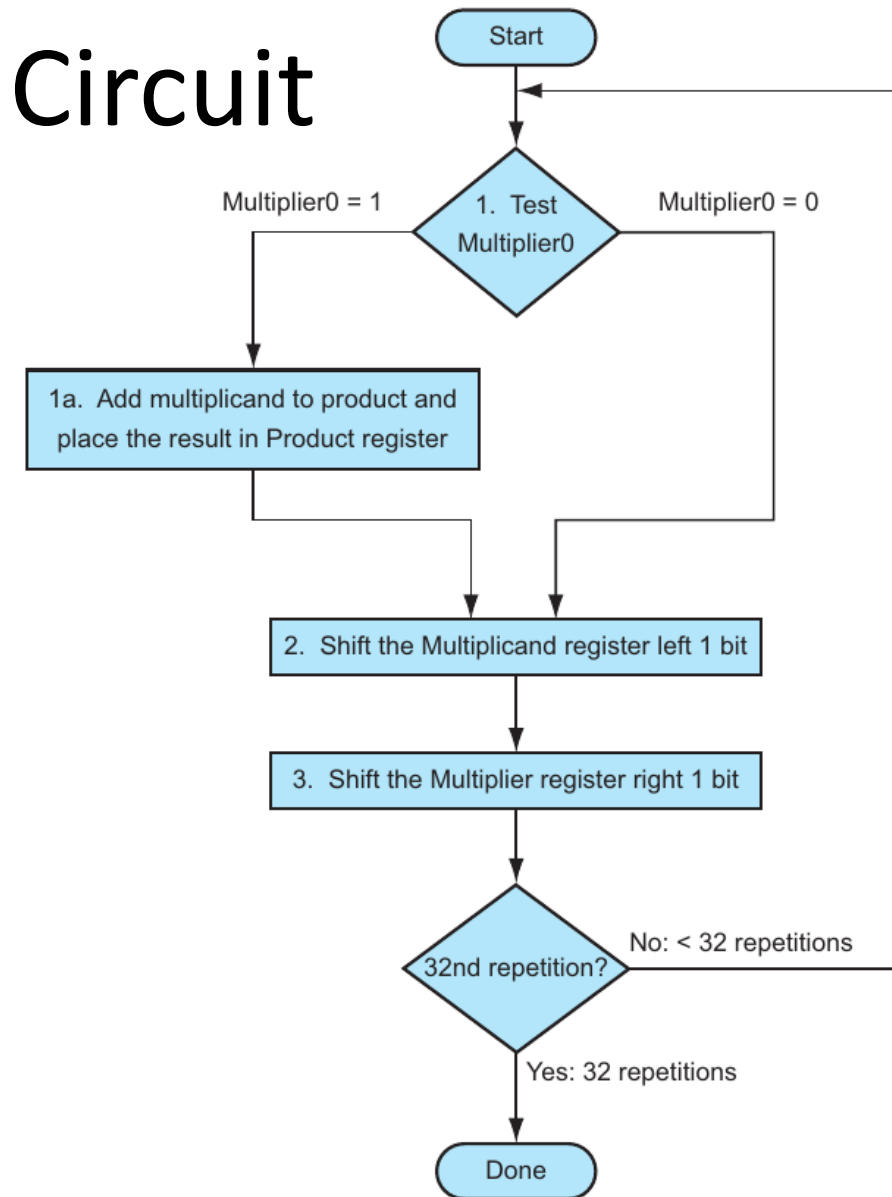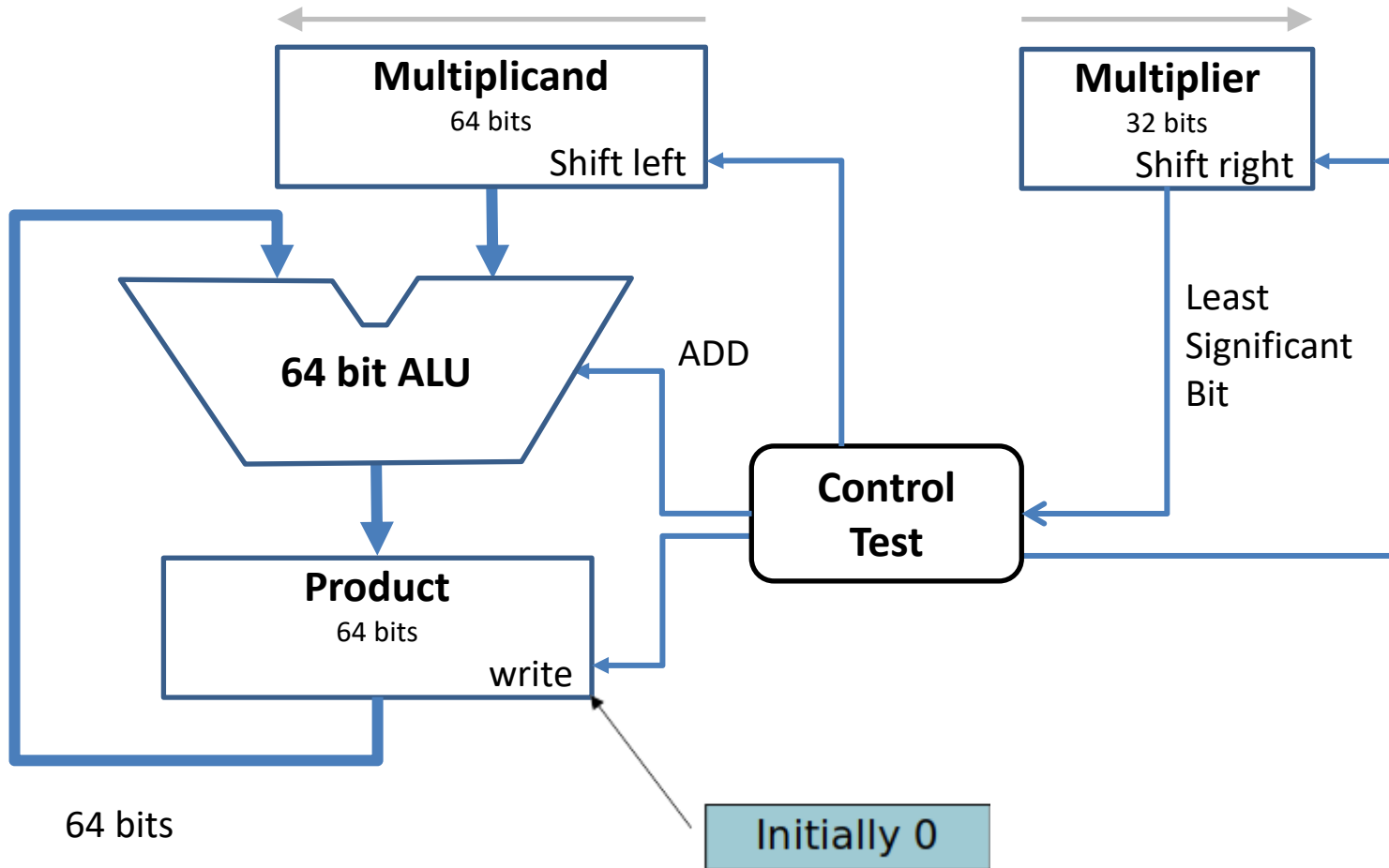



Repeat, shifting 32 times! Good enough? How is this wasteful?

Simple Multiplication Circuit

4-bit Example
 Multiplicand: 0010
 Multiplier: 0011
 Repetition: 4

Iteration	Step	Multiplier	Multiplicand	Product
0	Initial values	001 <u>1</u>	0000 0010	0000 0000
1	1a: 1 \Rightarrow Prod = Prod + Mcand	0011	0000 0010	0000 0010
	2: Shift left Multiplicand	0011	0000 0100	0000 0010
	3: Shift right Multiplier	000 <u>1</u>	0000 0100	0000 0010
2	1a: 1 \Rightarrow Prod = Prod + Mcand	0001	0000 0100	0000 0110
	2: Shift left Multiplicand	0001	0000 1000	0000 0110
	3: Shift right Multiplier	000 <u>0</u>	0000 1000	0000 0110
3	1: 0 \Rightarrow No operation	0000	0000 1000	0000 0110
	2: Shift left Multiplicand	0000	0001 0000	0000 0110
	3: Shift right Multiplier	000 <u>0</u>	0001 0000	0000 0110
4	1: 0 \Rightarrow No operation	0000	0001 0000	0000 0110
	2: Shift left Multiplicand	0000	0010 0000	0000 0110
	3: Shift right Multiplier	0000	0010 0000	0000 0110

Simple Multiplication Circuit

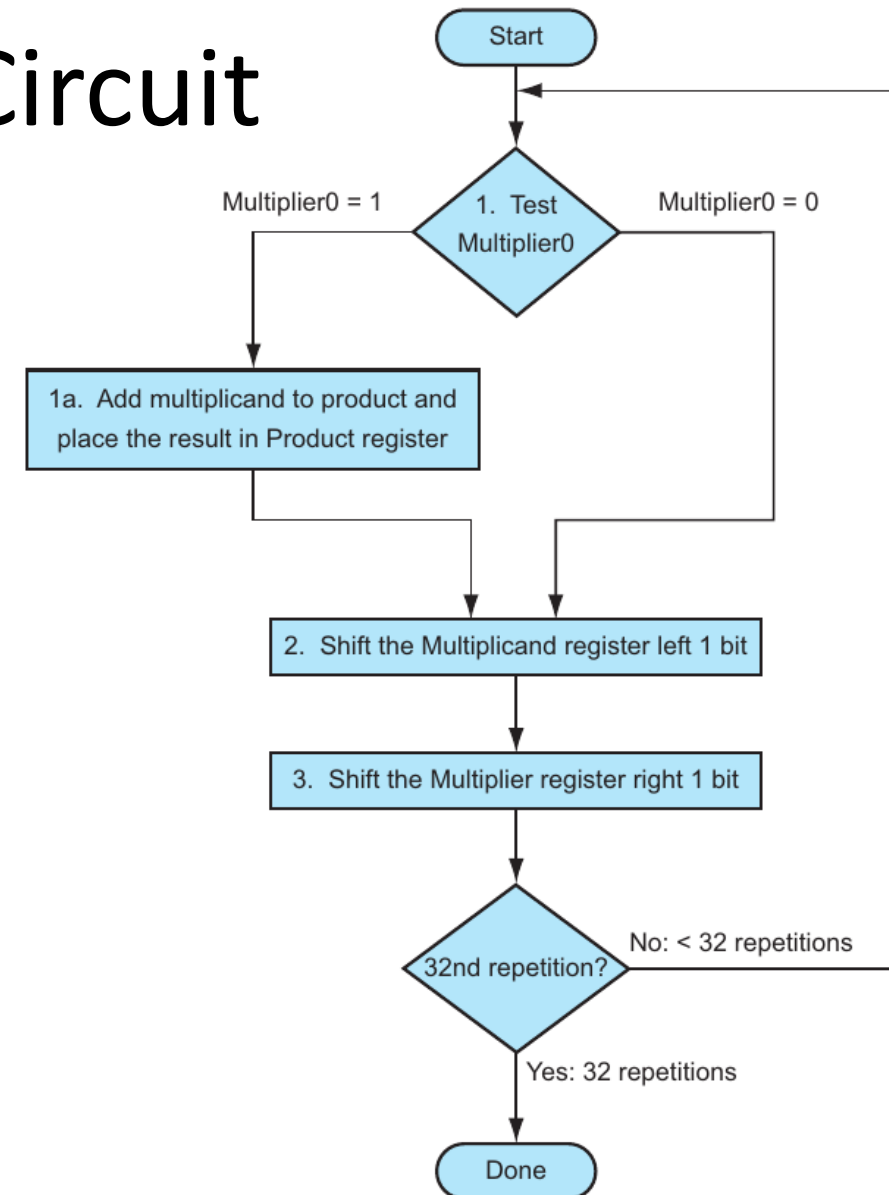 

Repeat, shifting 32 times! Good enough? How is this wasteful?

Refined Multiplication Circuit

4-bit Example

Multiplicand: 0010


Multiplier: 0011

Repetition: 4

Note that there is no shift left to the multiplicand as shifting right the product register at each step performs that alignment process.

Iteration	Step	Multiplicand	Product
0	Initial values	0010	0000 0011
1	Product= Product + Multiplicand	0010	0010 0011
	Shift right the product register	0010	0001 0001
2	Product= Product + Multiplicand	0010	0011 0001
	Shift right the product register	0010	0001 1000
3	Shift right the product register	0010	0000 1100
4	Shift right the product register	0010	0000 0110

Product Multiplier

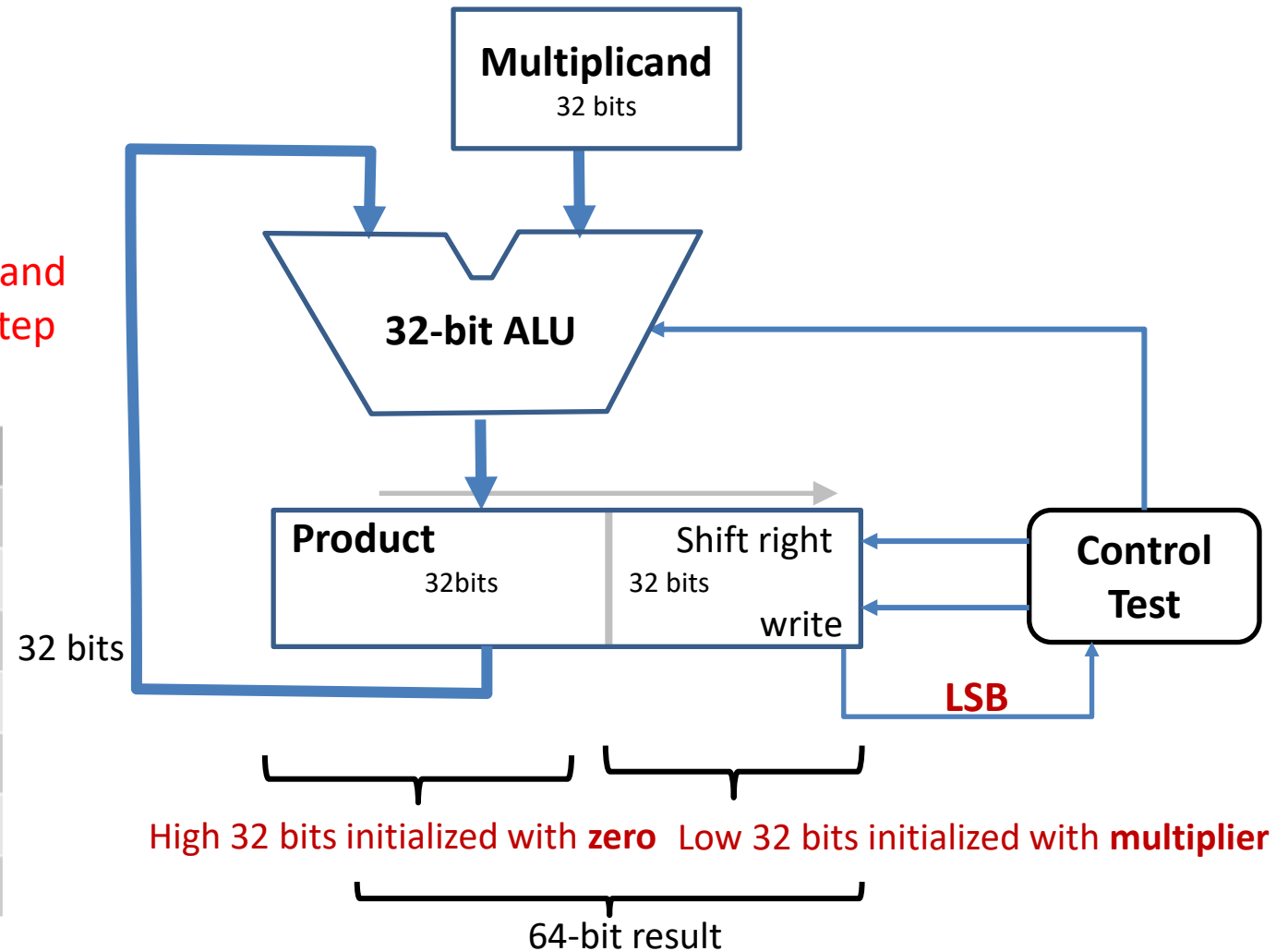


Signed Multiplication

- Convert the multiplier and the multiplicand to positive numbers and remember the original signs
- Multiply positive numbers
- The sign of the product is negative if the signs of the operands were different
- There are faster ways to do multiplication, but outside of scope of this course

Division


Division for Positive Numbers

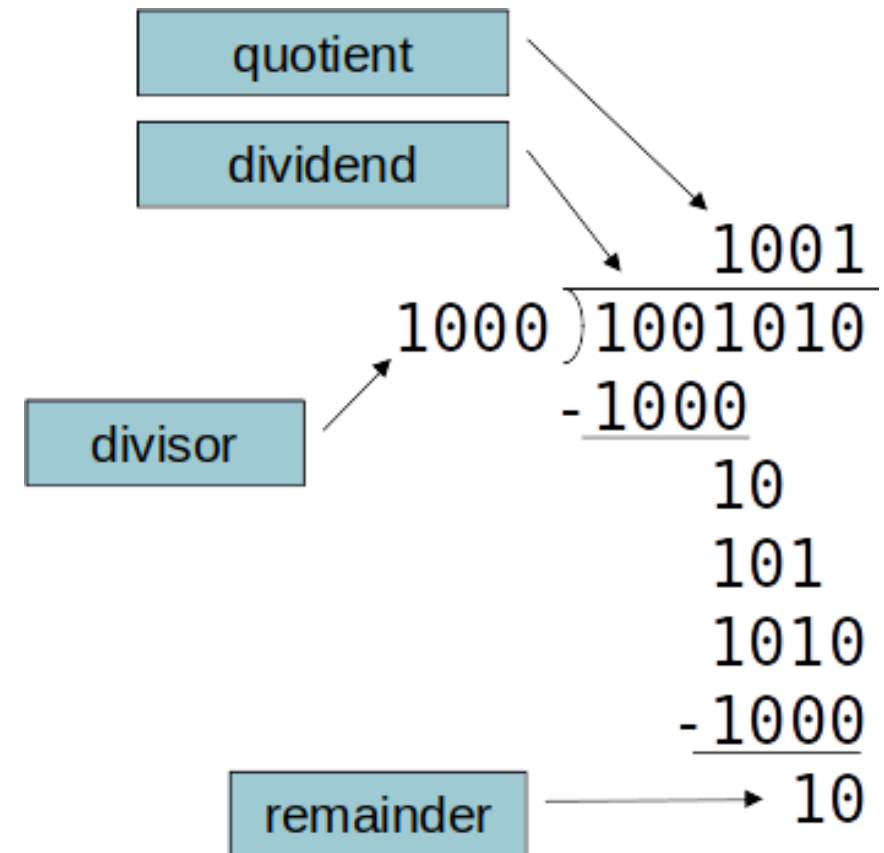- Binary division is similar, and in many respects easier!
- Approach
 - If divisor \leq dividend, 1 in quotient, subtract the divisor from the dividend
 - If divisor $>$ dividend, 0 in quotient, bring down next dividend bit




dividend / divisor = quotient, remainder

Division for Positive Numbers

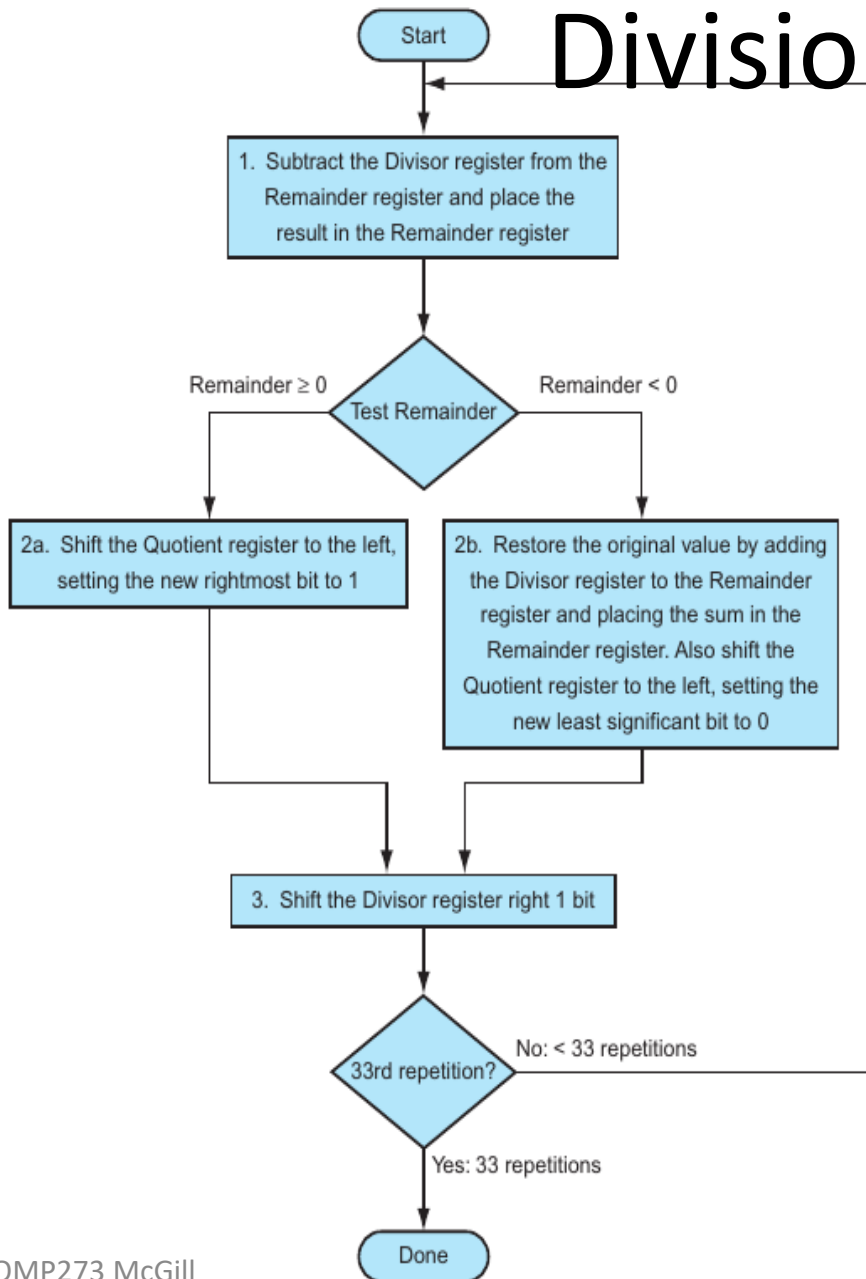


Initialize Divisor in **high word**, 0 in low word

Initialize Quotient with 0

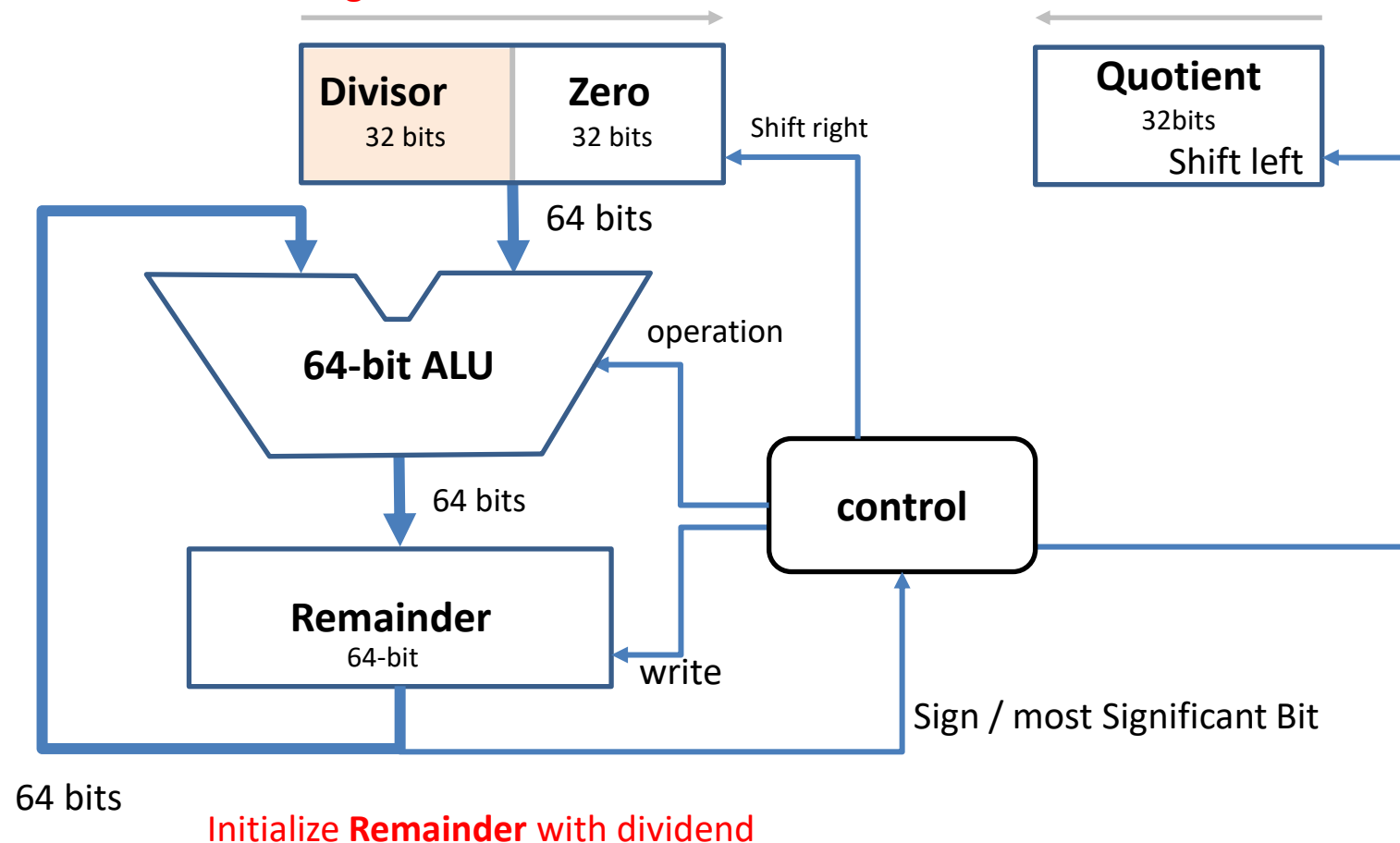


Division for Positive Numbers

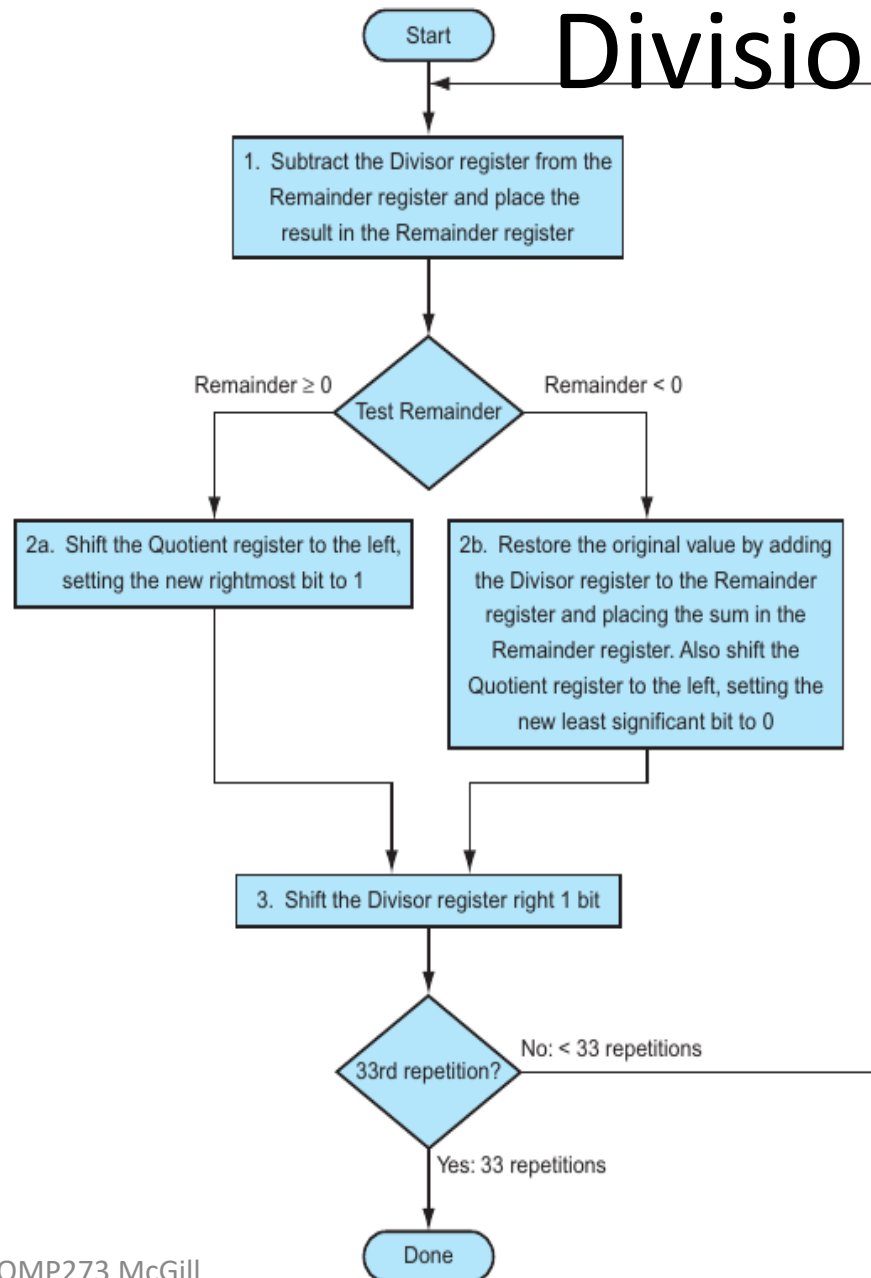4-bit Example
Dividend: 0111
Divisor: 0010
Repetition: 5



Initialize Divisor in **high word**, 0 in low word

Initialize Quotient with 0

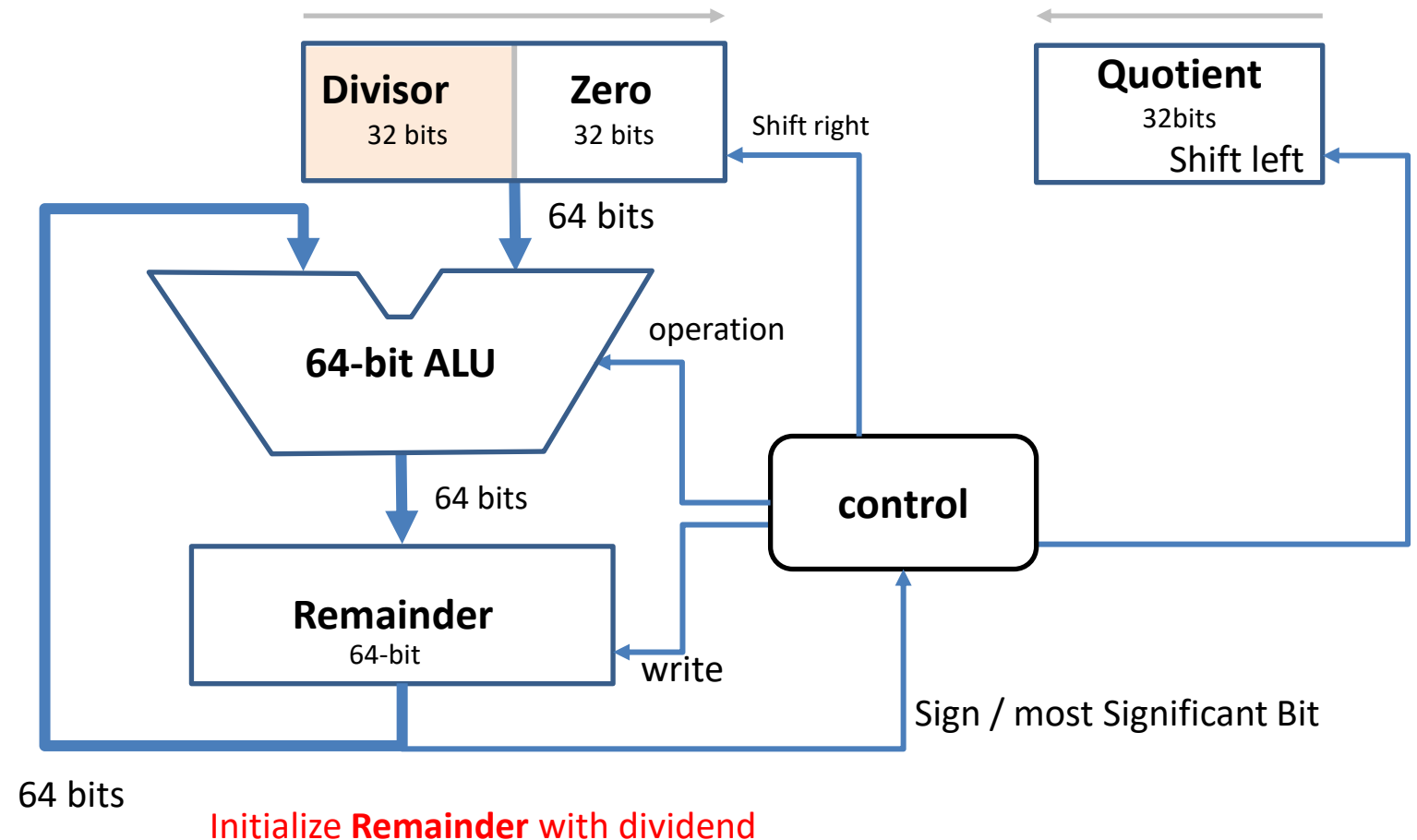

Division for Positive Numbers

4-bit Example

Dividend: 0111

Divisor: 0010

Repetition: 5 (i.e., $n+1$)

Iteration	Step	Quotient	Divisor	Remainder
0	Initial values	0000	0010 0000	0000 0111
1	1: $Rem = Rem - Div$	0000	0010 0000	0 110 0111
	2b: $Rem < 0 \Rightarrow +Div, sll Q, Q0 = 0$	0000	0010 0000	0000 0111
	3: Shift Div right	0000	0001 0000	0000 0111
2	1: $Rem = Rem - Div$	0000	0001 0000	0 111 0111
	2b: $Rem < 0 \Rightarrow +Div, sll Q, Q0 = 0$	0000	0001 0000	0000 0111
	3: Shift Div right	0000	0000 1000	0000 0111
3	1: $Rem = Rem - Div$	0000	0000 1000	0 111 1111
	2b: $Rem < 0 \Rightarrow +Div, sll Q, Q0 = 0$	0000	0000 1000	0000 0111
	3: Shift Div right	0000	0000 0100	0000 0111
4	1: $Rem = Rem - Div$	0000	0000 0100	0 000 0011
	2a: $Rem \geq 0 \Rightarrow sll Q, Q0 = 1$	0001	0000 0100	0000 0011
	3: Shift Div right	0001	0000 0010	0000 0011
5	1: $Rem = Rem - Div$	0001	0000 0010	0 000 0001
	2a: $Rem \geq 0 \Rightarrow sll Q, Q0 = 1$	0011	0000 0010	0000 0001
	3: Shift Div right	0011	0000 0001	0000 0001

Signed Division

- Simple solution
 - Divide using absolute values
 - Negate the quotient if the signs disagree
- What should be the sign of the remainder?

Dividend = Quotient * Divisor + Remainder


$$7/2 = 3 \text{ R } 1$$

$-7/2 = -3 \text{ R } -1$ (needs to be a negative remainder, otherwise ~~$-7/2 = -4 \text{ R } 1$~~)

Rule: Dividend and remainder must have the same signs

$$7/-2 = -3 \text{ R } 1$$

$$-7/2 = -3 \text{ R } -1$$

 

Review and more information

- Multiplication (Section 3.3)
- Division (Section 3.4)